



Gazi Üniversitesi  
Teknoloji Fakültesi  
Bilgisayar Mühendisliği Bölümü

## Sayısal Elektronik Devreler Laboratuvarı Final Sınav Ödevi

-Ders notunda verilen uygulamalar

Hazırlayan  
Özgür Sadık Utku  
181816072

# 11.HAFTA

## 11.1 Moore Makinaları

### Kod


```
22 :  
23 module ozgur_Moore(din,clk,reset,y);  
24     input din,clk,reset;  
25     output reg y;  
26     parameter S0=3'b000,S1=3'b001,S2=3'b010,S3=3'b011,  
27                 S4=3'b100,S5=3'b101,S6=3'b110,S7=3'b111;  
28     reg [2:0] gelecekDurum;  
29     always @(posedge clk)  
30     begin  
31         if(reset)  
32         begin  
33             gelecekDurum=S0;  
34             y=0;  
35         end  
36         else  
37         begin  
38             case(gelcekDurum)  
39             S0:begin  
40                 y=0;  
41                 if(din==0)  
42                     gelecekDurum=S1;  
43                 else  
44                     gelecekDurum=S0;  
45             end  
46             S1:begin  
47                 y=0;  
48                 if(din==0)  
49                     gelecekDurum=S2;  
50                 else  
51                     gelecekDurum=S3;  
52             end  
53             S2:begin  
54                 y=0;  
55                 if(din==0)  
56                     gelecekDurum=S4;  
57                 else  
58                     gelecekDurum=S3;  
59             end  
60             S3:begin  
61                 y=0;  
62                 if(din==0)  
63                     gelecekDurum=S5;  
64                 else  
65                     gelecekDurum=S0;  
66             end  
67             S4:begin
```

```


68      y=0;
69      if(din==0)
70      gelecekDurum=S4;
71      else
72      gelecekDurum=S6;
73      end
74      S5:begin
75      y=0;
76      if(din==0)
77      gelecekDurum=S2;
78      else
79      gelecekDurum=S7;
80      end
81      S6:begin
82      y=0;
83      if(din==0)
84      gelecekDurum=S5;
85      else
86      gelecekDurum=S0;
87      end
88      S7:begin
89      y=1;
90      if(din==0)
91      gelecekDurum=S5;
92      else
93      gelecekDurum=S0;
94      end
95  endcase
96  end
97 end
98 endmodule

```


## RTL Şematik

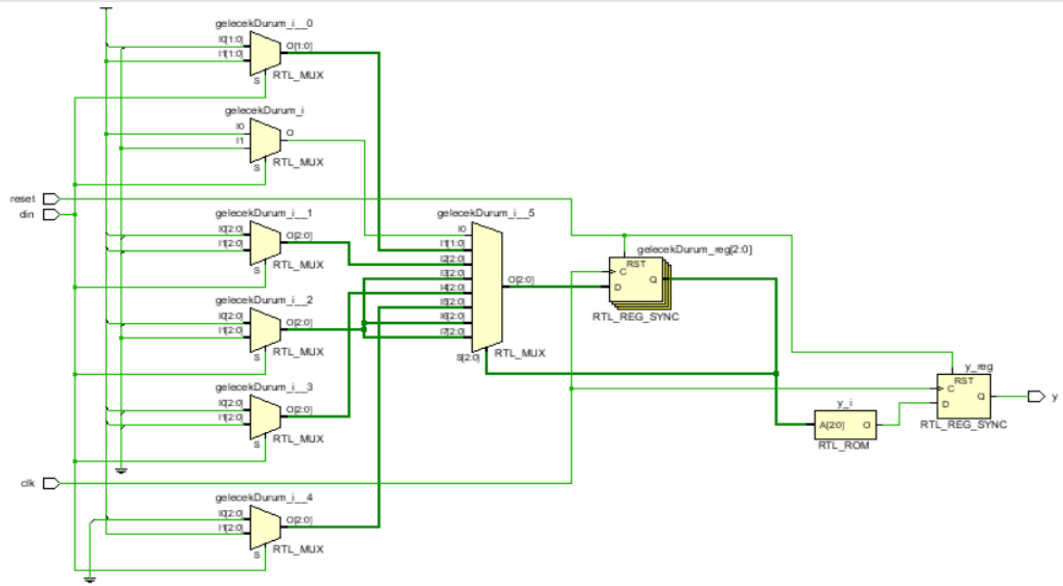


## Şematik

 

## IP Bloğu

 

## Similasyon Sonucu

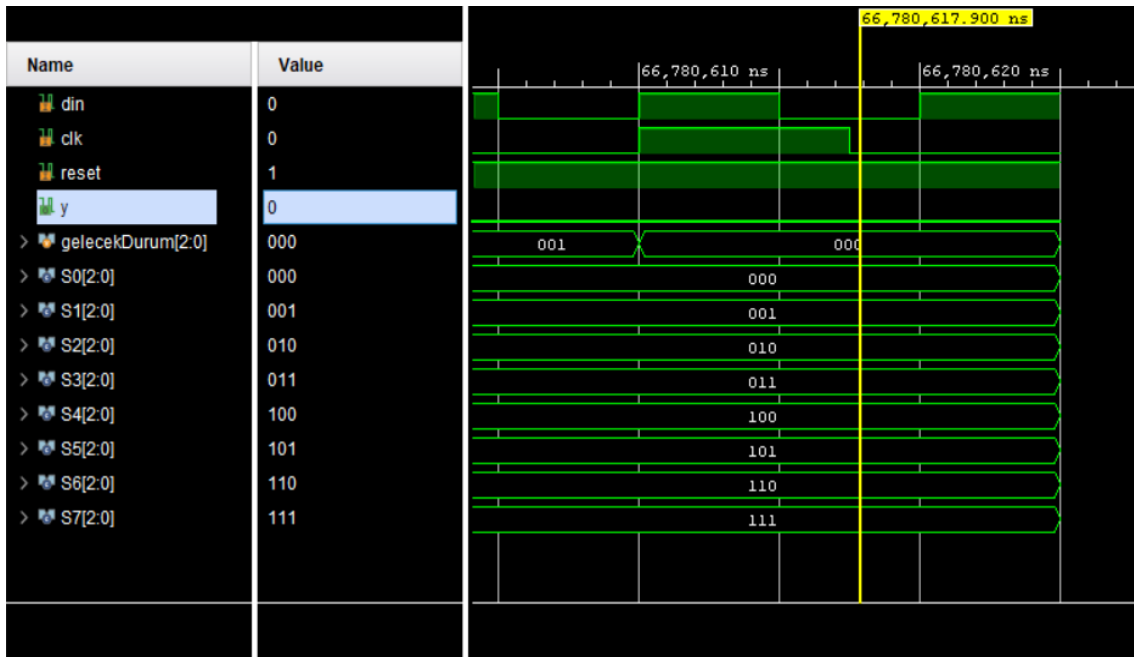

## 11.2 Mealy Makinaları

### Kod


```
22 :  
23 module ozgur_Mealy(din,clk,reset,y);  
24 input din,clk,reset;  
25 output reg y;  
26 parameter S0=3'b000,S1=3'b001,S2=3'b010,S3=3'b011,  
27           S4=3'b100,S5=3'b101;  
28 reg [2:0] gelecekDurum;  
29 always @(posedge clk)  
30 begin  
31     if(reset)  
32     begin  
33         gelecekDurum=S0;  
34         y=0;  
35     end  
36     else  
37     case (gelecekDurum)  
38     S0:begin  
39         if (din==0)  
40         begin  
41             gelecekDurum=S1;  
42             y=0;  
43         end  
44         else  
45         begin  
46             gelecekDurum=S0;  
47             y=0;  
48         end  
49         end  
50     S1:begin  
51         if (din==0)  
52         begin  
53             gelecekDurum=S3;  
54             y=0;  
55         end  
56         else  
57         begin  
58             gelecekDurum=S2;  
59             y=0;  
60         end  
61         end  
62     S2:begin  
63         if (din==0)  
64         begin  
65             gelecekDurum=S5;  
66             y=0;  
67         end  
68         else  
69         begin  
70             gelecekDurum=S0;  
71             y=0;  
72         end  
73         end  
74     S3:begin  
75         if (din==0)  
76         begin  
77             gelecekDurum=S4;  
78             y=0;  
79         end  
80         else  
81         begin  
82             gelecekDurum=S1;  
83             y=0;  
84         end  
85         end  
86     S4:begin  
87         if (din==0)  
88         begin  
89             gelecekDurum=S0;  
90             y=0;  
91         end  
92         else  
93         begin  
94             gelecekDurum=S2;  
95             y=0;  
96         end  
97         end  
98     S5:begin  
99         if (din==0)  
100        begin  
101            gelecekDurum=S3;  
102            y=0;  
103        end  
104        else  
105        begin  
106            gelecekDurum=S4;  
107            y=0;  
108        end  
109        end  
110    end  
111 end  
112
```

```


68      else
69      begin
70      gelecekDurum=S0;
71      y=0;
72      end
73      end
74      S3:begin
75      if(din==0)
76      begin
77      gelecekDurum=S4;
78      y=0;
79      end
80      else
81      begin
82      gelecekDurum=S2;
83      y=0;
84      end
85      end
86      S4:begin
87      if(din==0)
88      begin
89      gelecekDurum=S4;
90      y=0;
91      end
92      else
93      begin
94      gelecekDurum=S2;
95      y=1;
96      end
97      end
98      S5:begin
99      if(din==0)
100     begin
101     gelecekDurum=S3;
102     y=0;
103     end
104     else
105     begin
106     gelecekDurum=S2;
107     y=0;
108     end
109     end
110     endcase
111 end
112 endmodule

```


## RTL Şematik

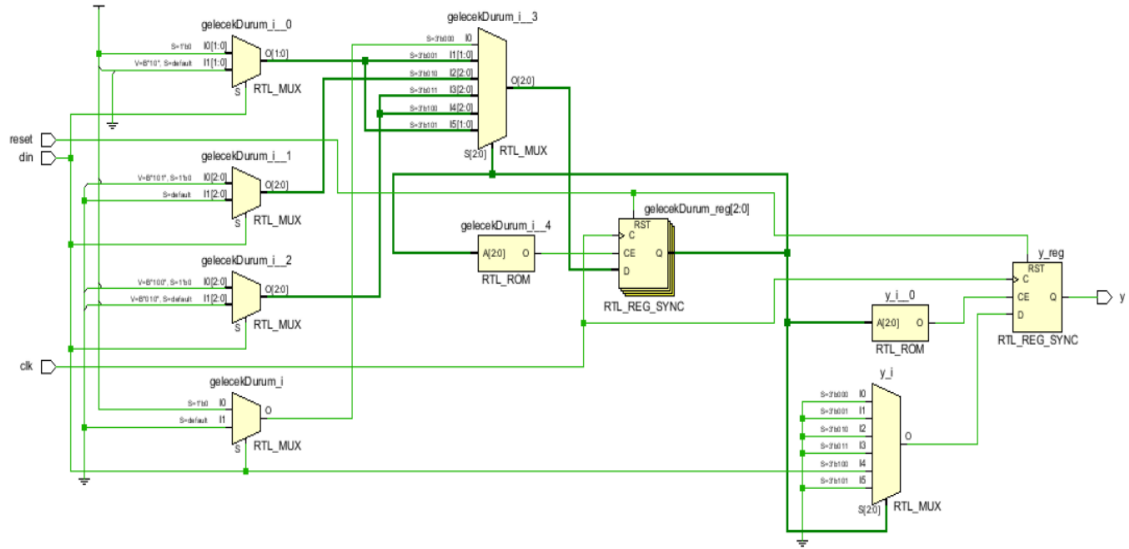


## Şematik

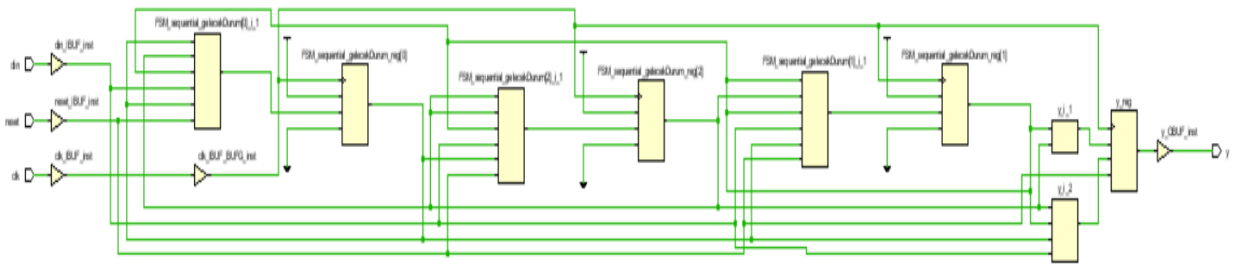

## IP Bloğu

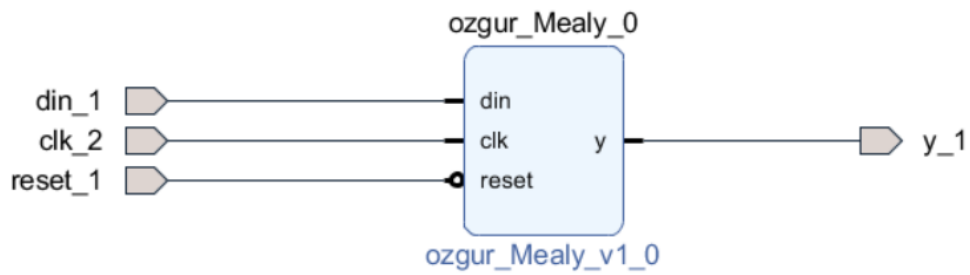

## Similasyon Sonucu

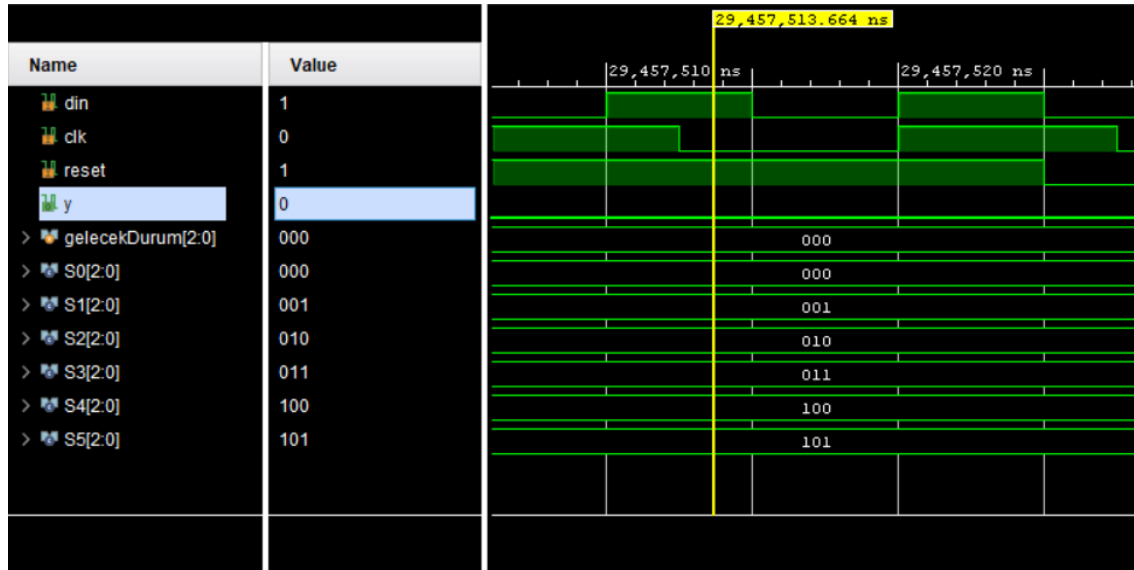

## 12.HAFTA

### 12.1 FIFO(First In First Out)

#### Kod

```
22 :  
23 module ozgur_FIFO(Clk,dataIn,RD,WR,EN,  
24 dataOut,Rst,bos,dolu);  
25 input Clk,RD,WR,EN,Rst;  
26 output bos,dolu;  
27 input [31:0] dataIn;  
28 output reg [31:0] dataOut;  
29 reg[2:0] Sayac=0;  
30 reg [31:0] FIFO [0:7];  
31 reg [2:0] okumaSayaci=0,yazmaSayaci=0;  
32 assign bos =(Sayac==0) ? 1'b1:1'b0;  
33 assign dolu =(Sayac==8) ? 1'b1:1'b0;  
34 always@(posedge Clk)  
35 begin  
36 if(EN==0);  
37 else begin  
38 if(Rst) begin  
39 okumaSayaci=0;  
40 yazmaSayaci=0;  
41 end  
42 else if(RD==1'b1 && Sayac!=0) begin  
43 dataOut=FIFO[okumaSayaci];  
44 okumaSayaci=okumaSayaci+1;
```




```


45 end
46 else if (WR==1'b1 && Sayac<8) begin
47     FIFO[yazmaSayaci] = dataIn;
48     yazmaSayaci= yazmaSayaci+1;
49 end
50 else;
51 end
52 if(yazmaSayaci==8)
53     yazmaSayaci=0;
54 else if(okumaSayaci==8)
55     okumaSayaci=0;
56 else;
57 if(okumaSayaci>yazmaSayaci) begin
58     Sayac=okumaSayaci-yazmaSayaci;
59 end
60 else if(yazmaSayaci>okumaSayaci)
61     Sayac=yazmaSayaci-okumaSayaci;
62 else;
63 end
64 endmodule

```


## RTL Şematik

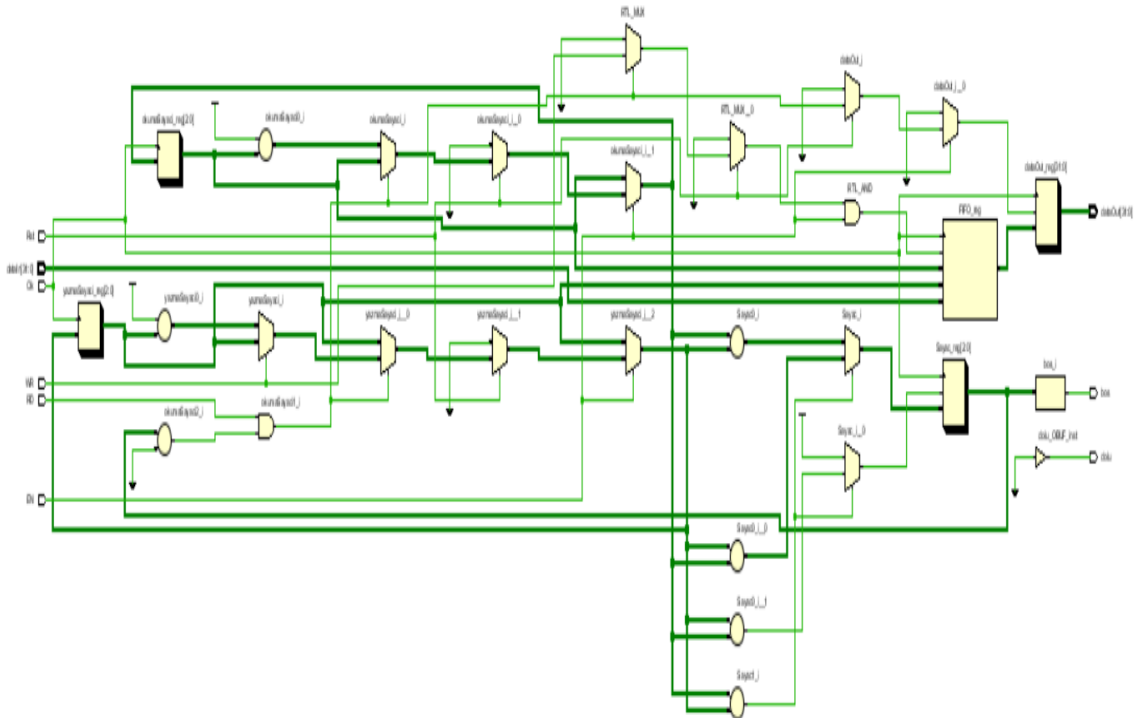


# Şematik

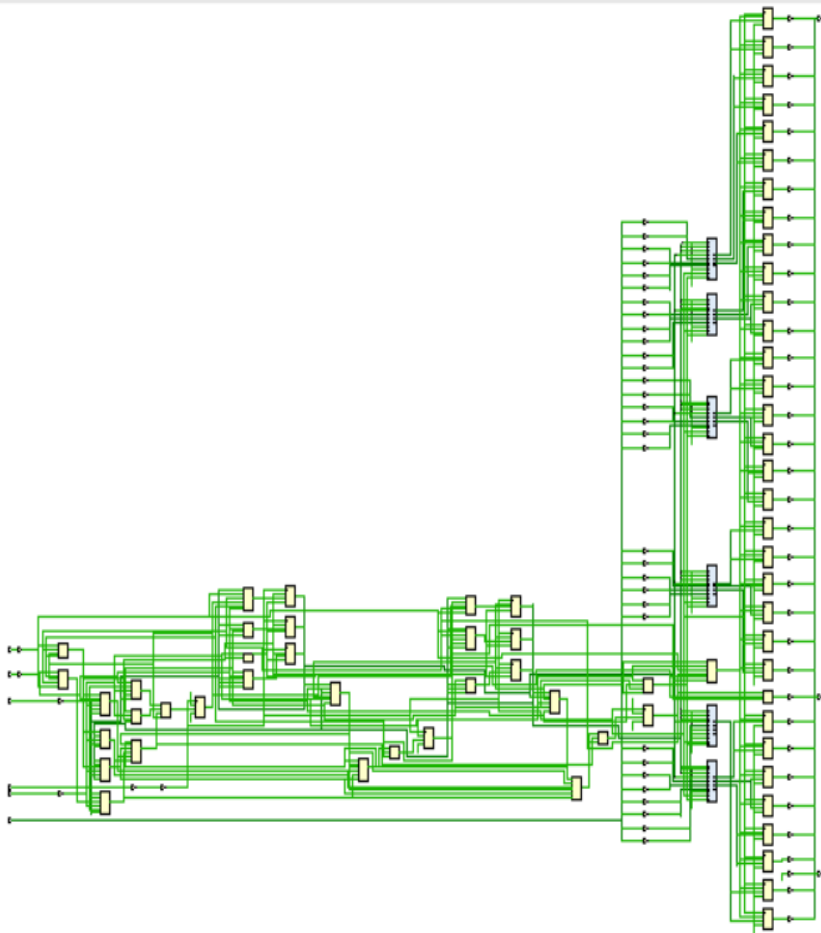

# IP Bloğu

 

# Similasyon Sonucu

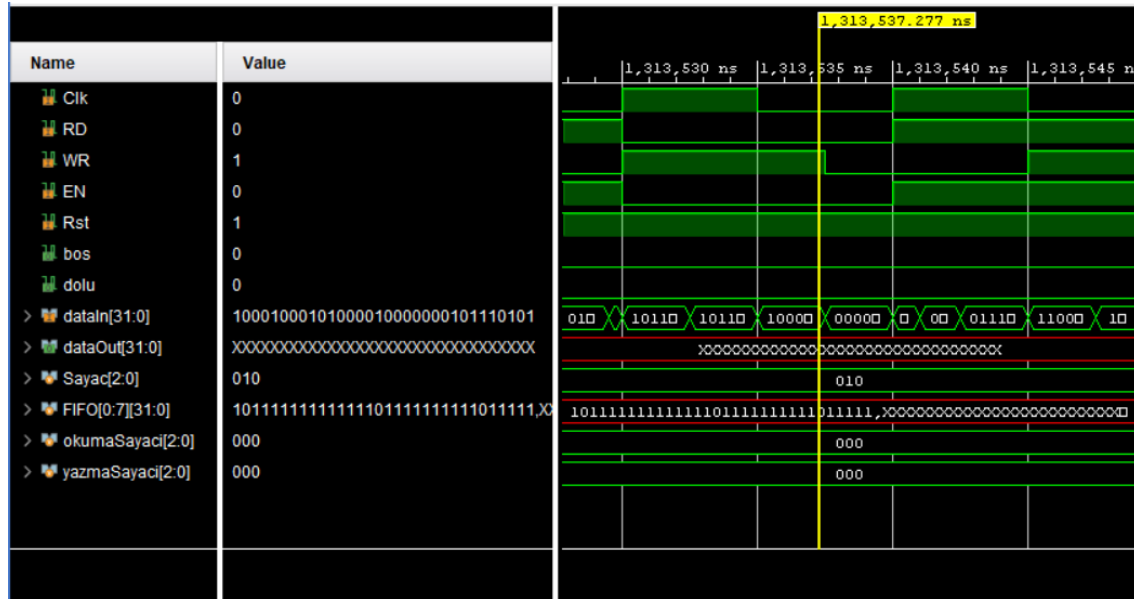

## 13.HAFTA

### 13.1 Trafik Işığı

#### Kod

```
22 :
23 module ozgur_trafik_isigi(light_highway, light_farm, C, clk, rst_n);
24 parameter HGRE_FRED=2'b00, // Highway green and farm red
25           HYEL_FRED = 2'b01, // Highway yellow and farm red
26           HRED_FGRE=2'b10, // Highway red and farm green
27           HRED_FYEL=2'b11; // Highway red and farm yellow
28 input C, // sensor
29        clk, // clock = 50 MHz
30        rst_n; // reset active low
31 output reg[2:0] light_highway, light_farm; // output of lights
32 // fpga4student.com FPGA projects, VHDL projects, Verilog projects
33 reg[27:0] count=0,count_delay=0;
34 reg delay10s=0, delay3s1=0,delay3s2=0,RED_count_en=0,YELLOW_count_en1=0,YELLOW_count_en2=0;
35 wire clk_enable; // clock enable signal for 1s
36 reg[1:0] state, next_state;
37 // next state
38 always @(posedge clk or negedge rst_n)
39 begin
40 if(~rst_n)
41     state <= 2'b00;
42 else
43     state <= next_state;
44 end
```

```

45 // FSM
46 always @(*)
47 begin
48 case(state)
49 HGRE_FRED: begin // Green on highway and red on farm way
50     RED_count_en=0;
51     YELLOW_count_en1=0;
52     YELLOW_count_en2=0;
53     light_highway = 3'b001;
54     light_farm = 3'b100;
55     if(C) next_state = HYEL_FRED;
56     // if sensor detects vehicles on farm road,
57     // turn highway to yellow -> green
58     else next_state =HGRE_FRED;
59 end
60 HYEL_FRED: begin// yellow on highway and red on farm way
61     light_highway = 3'b010;
62     light_farm = 3'b100;
63     RED_count_en=0;
64     YELLOW_count_en1=1;
65     YELLOW_count_en2=0;
66     if(delay3s1) next_state = HRED_FGRE;
67     // yellow for 3s, then red
68     else next_state = HYEL_FRED;
69 end
70 HRED_FGRE: begin// red on highway and green on farm way
71     light_highway = 3'b100;
72     light_farm = 3'b001;
73     RED_count_en=1;
74     YELLOW_count_en1=0;
75     YELLOW_count_en2=0;
76     if(delay10s) next_state = HRED_FYEL;
77     // red in 10s then turn to yello -> green again for high way
78     else next_state =HRED_FGRE;
79 end
80 HRED_FYEL:begin// red on highway and yellow on farm way
81     light_highway = 3'b100;
82     light_farm = 3'b010;
83     RED_count_en=0;
84     YELLOW_count_en1=0;
85     YELLOW_count_en2=1;
86     if(delay3s2) next_state = HGRE_FRED;
87     // turn green for highway, red for farm road
88     else next_state =HRED_FYEL;
89 end
90 default: next_state = HGRE_FRED;


```

```


91 endcase
92 end
93 // fpga4student.com FPGA projects, VHDL projects, Verilog projects
94 // create red and yellow delay counts
95 always @(posedge clk)
96 begin
97     if(clk_enable==1) begin
98         if(RED_count_en||YELLOW_count_en1||YELLOW_count_en2)
99             count_delay <=count_delay + 1;
100         if((count_delay == 9)&&RED_count_en)
101             begin
102                 delay10s=1;
103                 delay3s1=0;
104                 delay3s2=0;
105                 count_delay<=0;
106             end
107         else if((count_delay == 2)&&YELLOW_count_en1)
108             begin
109                 delay10s=0;
110                 delay3s1=1;
111                 delay3s2=0;
112                 count_delay<=0;
113             end
114         else if((count_delay == 2)&&YELLOW_count_en2)
115             begin
116                 delay10s=0;
117                 delay3s1=0;
118                 delay3s2=1;
119                 count_delay<=0;
120             end
121         else
122             begin
123                 delay10s=0;
124                 delay3s1=0;
125                 delay3s2=0;
126             end
127         end
128     end
129     // create 1s clock enable
130     always @(posedge clk)
131     begin
132         count <=count + 1;
133         //if(count == 50000000) // 50,000,000 for 50 MHz clock running on real FPGA
134         if(count == 3) // for testbench
135             count <= 0;
136     end
137     assign clk_enable = count==3 ? 1: 0; // 50,000,000 for 50MHz running on FPGA
138 endmodule

```


## RTL Şematik

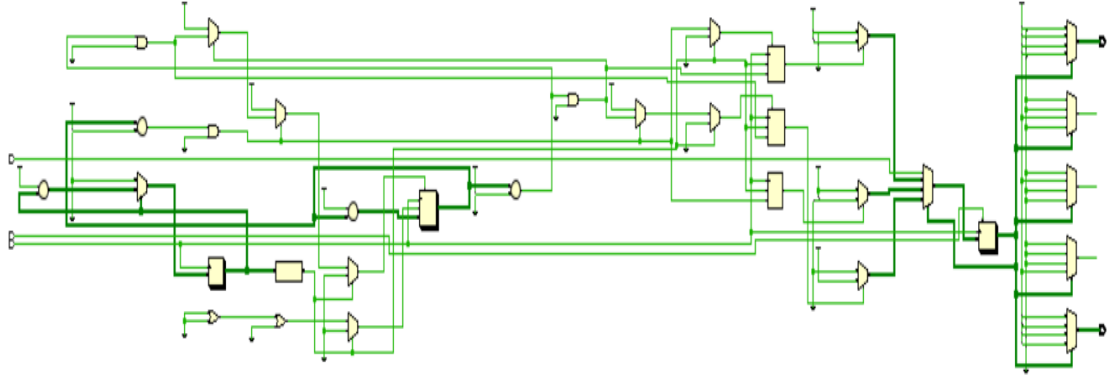

## Şematik

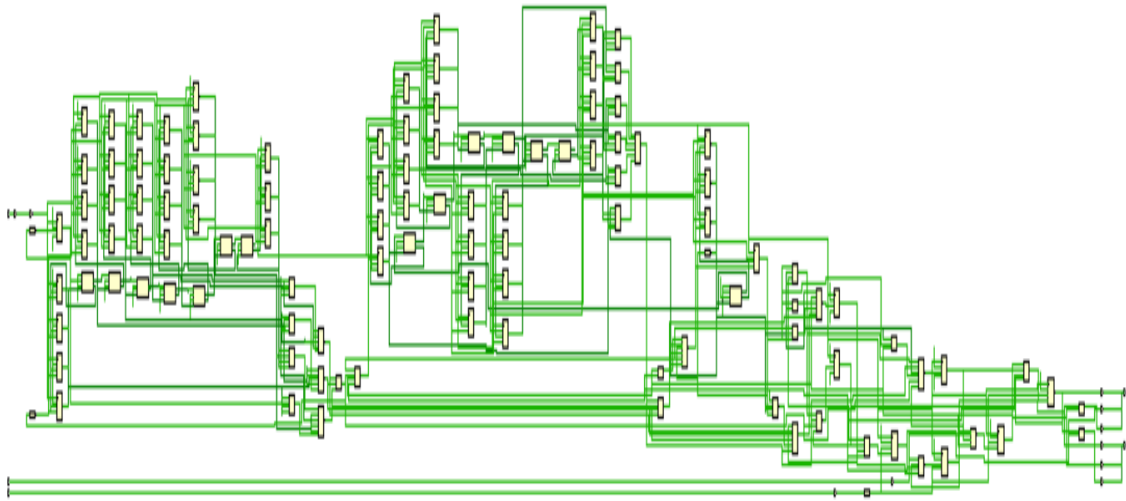

## IP Bloğu

 


## Similasyon Sonucu



# 15.HAFTA


## IP Bloğu

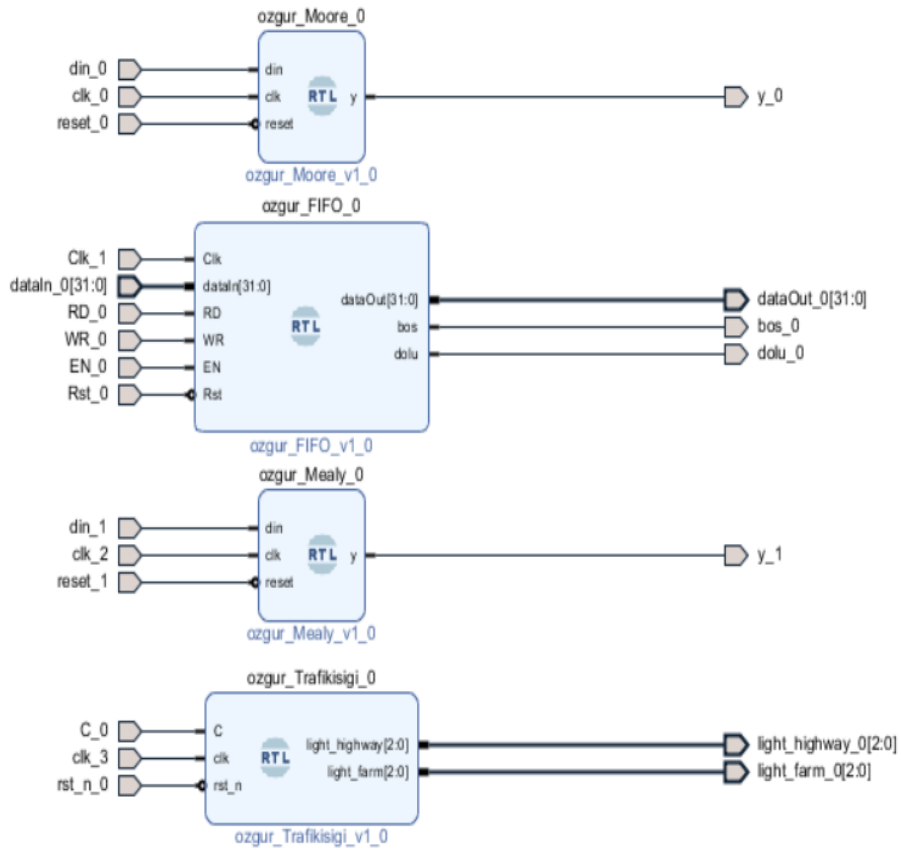




## IP Nasıl Kaydedilir

Yeni IP paketi oluşturulur.

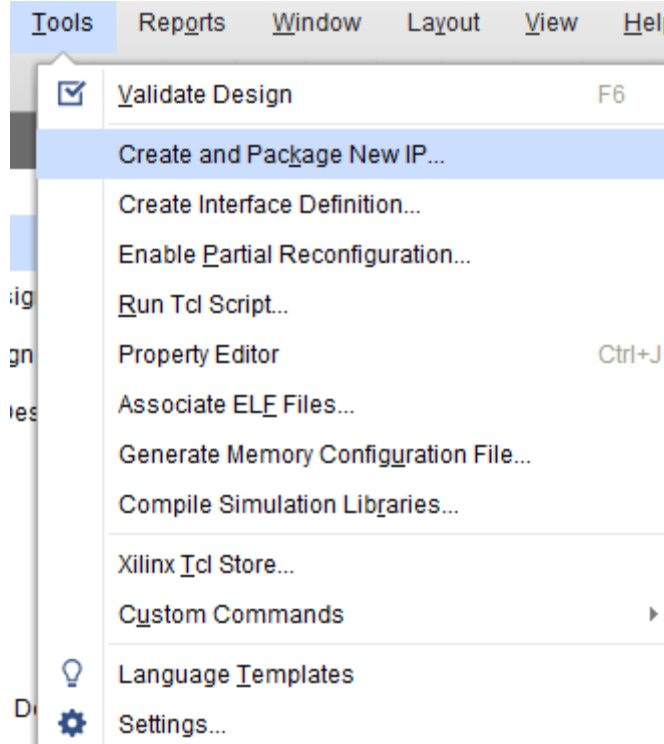

Next diyerek devam edilir.

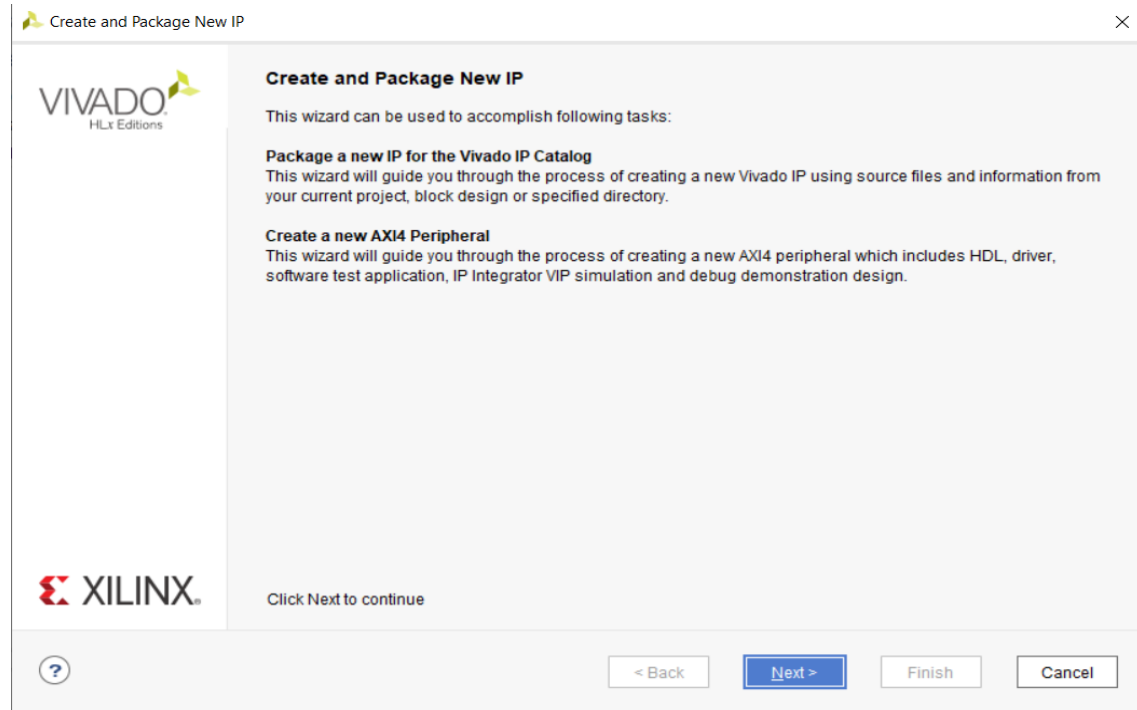

Package your current project seçilir ve next diyerek devam edilir

Create and Package New IP

**Create Peripheral, Package IP or Package a Block Design**

Please select one of the following tasks.

**Packaging Options**

☒ Package your current project  
Use the project as the source for creating a new IP Definition.

☐ Package a block design from the current project  
Choose a block design as the source for creating a new IP Definition.  
Select a block design: design\_1

☐ Package a specified directory  
Choose a directory as the source for creating a new IP Definition.

**Create AXI4 Peripheral**

☐ Create a new AXI4 peripheral  
Create an AXI4 IP, driver, software test application, IP Integrator AXI4 VIP simulation and debug demonstration design.

? < Back Next > Finish Cancel

Include xci files seçeneği seçilir ve next diyerek devam edilir.

Create and Package New IP

**Package Your Current Project**

Select the directory where the IP Definition will be created and the associated options for packaging the current project.

IP location: c:/users/ozgur/ozgur\_fifo/ozgur\_fifo.srcs/sources\_1/new


**Packaging IP in the project**

☒ Include .xci files

☐ Include IP generated files

? < Back Next > Finish Cancel

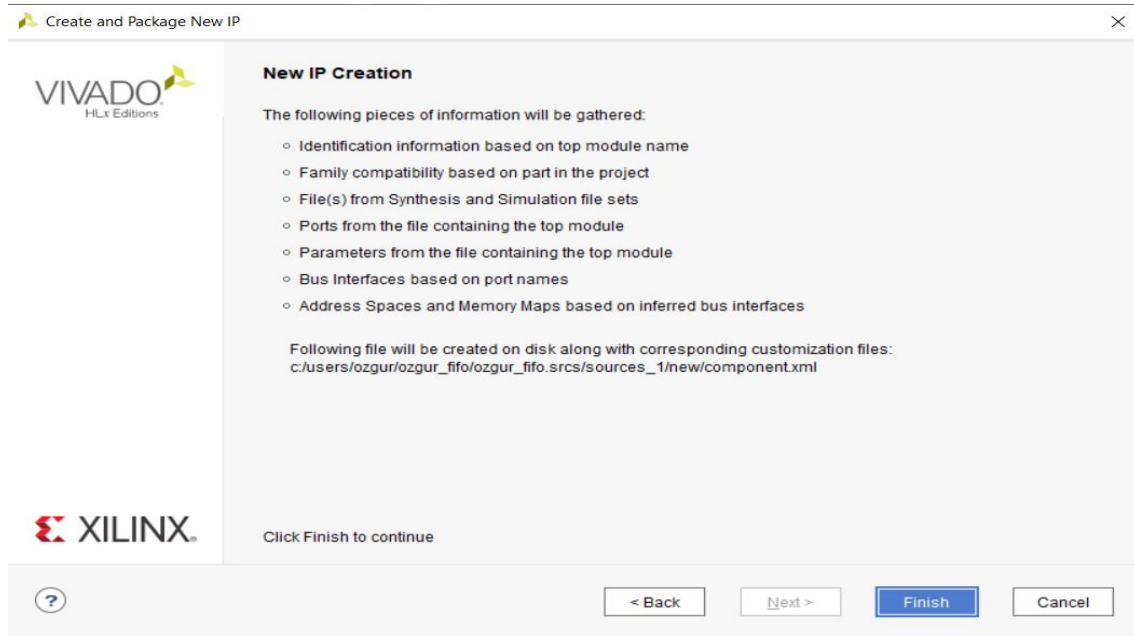Finish butonuna basilarak IP oluřturulması tamamlanır.



Açılan pencerede “Review and Package” bölümünden “Package IP” yapılır ve kaydedilir.

